



Examination : B.Tech. Semester- II (CE/IT/EC)

Seat No. :

Date : 25/04/2023

Day : Tuesday

Time : 08:30 to 09:45 AM

Max. Marks : 36

INSTRUCTIONS:

1. Figures to the right indicate maximum marks for that question.
2. The symbols used carry their usual meanings.
3. Assume suitable data, if required & mention them clearly. ($K = 1.380649 \times 10^{-23}$ joule per kelvin, Temp. $T = 300$ K, $h = 6.626 \times 10^{-34}$ J Hz⁻¹, $q = 1.602176634 \times 10^{-19}$ coulomb)
4. Draw neat sketches wherever necessary.

Q.1 Do as directed.

- CO1 U (a) Draw the schematic diagram of common anode seven segment display for displaying numerical digit 2. [12]
[2]
- CO2 A (b) Consider the following specification for the base biased CE configuration, $V_{CE(\text{Cut-off})} = 15$ V and $I_{C(\text{Sat})} = 5$ mA, Calculate the value of Collector Resistance (R_C). [2]
- CO1 U (c) Which of the following is true for LASER, [1]
(I) It produces coherent light (II) It produces light waves which are in phase with each other (III) It produces Intense focused beam of light (IV) All of above
- CO2 U (d) The fact that there are many free electrons in a transistor emitter region means the emitter is _____. [1]
(I) Lightly Doped (II) Heavily Doped (III) Un-doped (IV) Less Area
- CO4 U (e) Why does responsivity get reduce above cut-off wavelength in photo-detectors? [2]
- CO5 U (f) How fiber optic communication is advantageous over microwave communication? [2]
- CO5 U (g) Why does repeater required in optical fiber communication? [2]

Q.2 Attempt Any TWO from the following questions.

- CO2 E (a) Draw the schematic of base biased CE configuration with the following specifications: $R_B = 700\text{K}\Omega$, $R_C = 2\text{K}\Omega$, $V_{CC} = 12\text{V}$, $V_{BB} = 10\text{V}$, $\beta_{dc} = 100$. Calculate (I) I_C (II) V_{CE} (III) Sketch Load line for the same. (IV) Comment on the location of Q-Point on load line with the following options (Almost at the middle of load line, Towards cutoff point, Towards saturation point). [12]
(Note: Consider Second approximation of silicon NPN transistor) [6]
- CO2 E (b) Consider a base biased BJT circuit with $V_{BB} = 15\text{V}$, $V_{CC} = 25\text{V}$, $R_B = 23\text{K}\Omega$, $R_C = 2.3\text{K}\Omega$, $\beta_{dc} = 110$. Determine whether the transistor is saturated? Use (1) Saturation current method and (2) Collector -Voltage method to recognize the saturation. Also, calculate the saturated current gain. Consider the silicon NPN transistor with second approximation. [6]
- CO2 E (c) Draw the schematic of emitter biased CE configuration with the following specifications: $R_E = 1.8\text{K}\Omega$, $R_C = 1\text{K}\Omega$, $V_{CC} = 12\text{V}$, $V_{BB} = 5\text{V}$, $\beta_{dc} = 50$. Calculate (I) I_C (II) V_{CE} (III) Sketch Load line for the same. (IV) Comment on the location of Q-Point on load line with the following options (Almost at the middle of load line, Towards cutoff point, Towards saturation point). [6]
(Note: Consider Second approximation of silicon NPN transistor)

Q.3 Attempt the following questions.

- CO4 N (a) A p-i-n photo-diode, on an average, generates one- EHP per two incident photons at a wavelength of $0.85 \mu\text{m}$. Assuming all the photo-generated electrons are collected, calculate [12]
(i) the quantum efficiency of the diode; [6]
(ii) the maximum possible band gap energy in eV of the semiconductor, assuming the incident wavelength to be a long wavelength cut-off and
(iii) the mean output photo current when the incident optical power is $10 \mu\text{W}$.

- CO1 E (b) For the circuit shown in Fig-1 (I) Is the zener diode operating in breakdown region? (II) Calculate Zener Current (III) Calculate Load Current (Note: Consider Zener Diode with Ideal Approximation) [4]
- CO2 A (c) State True/False with mathematical equation "The slope of load line for emitter biased CE configuration is directly proportional to $\frac{1}{R_C + R_E}$ ". [2]

OR

- Q.3 Attempt the following questions. [12]
- CO4 N (a) (I) An APD has a quantum efficiency of 40% at $1.3 \mu\text{m}$ when illuminated with optical power of $0.3 \mu\text{W}$ at this wavelength, it produces an output photo current of $6 \mu\text{A}$ after avalanche gain. Calculate the multiplication factor of the diode. [4]
- (II) Calculate the responsivity of an ideal p-n photo diode at $1.55 \mu\text{m}$ wavelengths. (consider quantum efficiency = 1) [2]
- CO1 E (b) For the circuit shown in Fig-2 (I) Is the zener diode operating in breakdown region? (II) Calculate Zener Current (III) Calculate Load Current (Note: Consider Zener Diode with Ideal Approximation) [4]
- CO2 A (c) Derive the relationship between dc alpha (α) and Current gain (β) for BJT. [2]

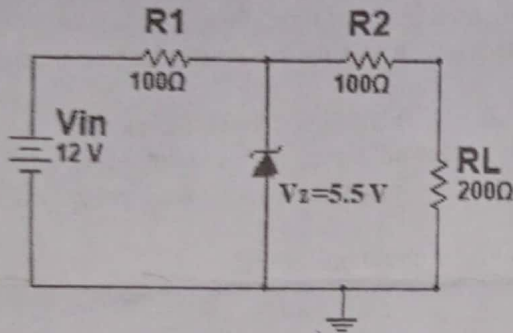


Fig.-1 (Q.3(b))

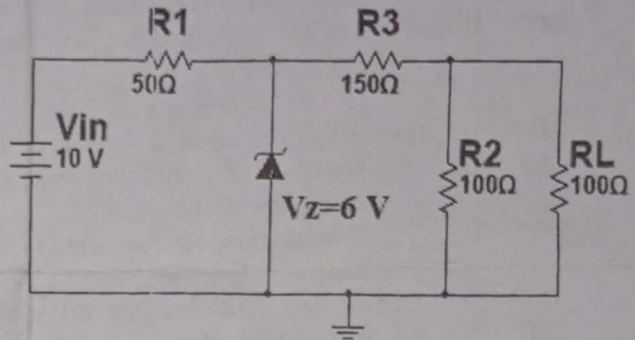


Fig.-2 (Q.3 (b) OR)

Blooms Taxonomy levels : R-Remembering, U- Understanding, A-Applying, N-Analyzing, E- Evaluating, C-Creating