



DHARMSINH DESAI UNIVERSITY, NADIAD
FACULTY OF TECHNOLOGY
B.TECH. SEMESTER III [COMPUTER ENGINEERING]
SUBJECT: (CE318) NAME: DESIGN OF DIGITAL CIRCUITS

Examination : Regular
Date : 08/11/2023
Time : 10.00 to 1.00 pm

Seat No :
Day : Wednesday
Max. Marks : 60


INSTRUCTIONS:

1. Answer each section in a separate answer book.
2. Figures to the right indicate maximum marks for that question.
3. The symbols used carry their usual meanings.
4. Assume suitable data, if required & mention them clearly.
5. Draw neat sketches wherever necessary.

SECTION - I

 
Q.1 Do as directed.

- CO1 C (a) Let r denote the number system radix. The only value(s) of r that satisfy the equation $\sqrt{121}_r = 11_r$ is? [10]
CO2 A (b) Show the advantage of $(r-1)$'s complement over r 's complement with an example. [2]
CO2 E (c) For an n -variable Boolean function how many maximum prime implicants are possible? [2]
CO3 U (d) The size of the ROM needed to implement a 4 bit multiplier is? [2]
CO4 N (e) The outputs of the two flip-flops Q1, Q2 in the figure shown are initialized to 0, 0. What is the sequence generated at Q1 upon application of clock signal? [2]



Q.2 Attempt Any TWO from the following questions.

CO2 C (a)

 


For the circuit shown in the above figure, determine the output of MUX 2 with steps. Show applications of the multiplexer.

- CO2 C (b) Design a 4-to-1 multiplexer using 2-to-4 Decoder. Support with the truth table and boolean expressions. [5]
CO2 C (c) Design a single combinational circuit for converting BCD to 2421 code using encoders and decoders. Also construct the truth table. [5]

 Q3. Attempt the following:

- CO3 A (a) Design a mod-6 counter with the sequence 10,11,12,13,14,15 using a binary counter with parallel load MSI. Show the steps with a state table, and a diagram. [10]
CO4 N (b) Show the State table, counting logic, state diagram and timing diagram of the counter shown in the below figure. [5]




OR

[10]

 Q3. Attempt the following:


- CO3 A (a) Design a 3-bit Synchronous Counter which can count odd and even sequences in a single circuit based on Mode Input M. Show the steps with a state table, and a diagram. [5]
- CO4 N (b) The below figure shows a binary counter with synchronous clear input. Determine the mod counting performed by the counter. Show the State table, counting logic, state diagram and timing diagram of the counter. [5]



Q.4 Do as directed.

CO3 N (a)

SECTION - II

 

[10]


[2]

Analyze the circuit shown in the above figure, the output required is $Y = AB + C'D'$. Determine the gates G1 and G2 which will result in the expression Y.

- CO3 N (b) Analyze the total number of self dual functions with n variables (with example). [2]
- CO1 E (c)

[2]

[2]

 


Describe the functionality achieved by the circuit shown in the above figure.

- CO4 U (d) Explain the difference between Flip flop and a latch. [2]
- CO1 A (e) Apply the concept of Edge triggering and level triggering with their respective applications. [2]
- Q.5 Attempt Any TWO from the following questions. [10]

- CO2 C (a) Design the circuit which converts a full adder to full-subtractor, derive the equations. [5]
- CO2 C (b) Design the circuit for function $F = \sum m(0,1,3,7,8)$. Minimize it using Quine-McCluskey Technique. [5]
- CO2 C (c) Design the circuit for $F(a,b,c) = a'c + ac' + b'c$, showing the total number prime implicants, and Essential prime implicants. [5]

 Q.6 Attempt the following:

- CO3 N (a) A sequential circuit has two flip flops A and B, two inputs x and y and an output z. The flip flop functions and the circuit output function are as follows: $JA = xB + y'B'$, $KA = xy'B'$, $JB = xA'$, $KB = xy' + A$, and $Z = xyA + x'y'B$. Obtain the logic diagram, state table, state diagram, and state equations. [10]
- CO3 C (b) Design a synchronous counter using JK flip flop for the given State diagram. [5]



OR

Q.6 Attempt the following:

[10]

- CO3 N (a) The full adder receives two external inputs x and y; the third input z comes from the output of a D flip flop. The carry output is transferred to the flip flop every clock pulse. The external S output gives the sum of x,y, and z. Obtain the state table and state diagram of the sequential circuit. [5]
- CO3 C (b) Design a counter that counts the decimal according to 2421 code using T flip flops, with state table and state diagram. [5]

Bloom's Taxonomy levels: R-Remembering, U- Understanding, A-Applying, N-Analyzing, E- Evaluating, C-Creating