



DHARMSINH DESAI UNIVERSITY, NADIAD
FACULTY OF TECHNOLOGY
B.TECH SEMESTER-3 (CE)
FIRST SESSIONAL

SUBJECT: (CE-308) Design of Digital Circuits

Examination : First Sessional

Date : 02/08/2023

Time : 11.00 AM to 12.15 PM

Seat No. : 31

Day : Wednesday

Max. Marks : 36

INSTRUCTIONS:


1. Figures to the right indicate maximum marks for that question.
2. The symbols used carry their usual meanings.
3. Assume suitable data, if required & mention them clearly.
4. Draw neat sketches wherever necessary.

Q.1 Do as directed.

[12]

- R (a) Which one of the following circuits is NOT equivalent to a 2-input XNOR (exclusive NOR) gate? [2]

CO2

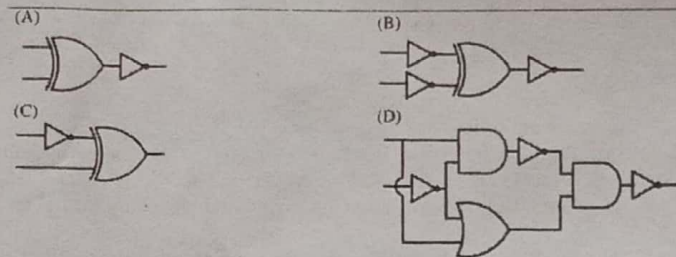


- CO2 U (b) Consider the following Boolean function of four variables: $f(w,x,y,z) = \sum(1,3,4,6,9,11,12,14)$. Which of the variable(s) is/are not impacting the function? [2]

- CO2 A (c) How many minimum number of gates are required to implement the Boolean function $(BC+D)$ if we have to use only 2-input NOR gates? Show the circuit. [2]

- CO2 A (d) $X = 01110$ and $Y = 11001$ are two 5-bit binary numbers represented in two's complement format. Determine the sum of X and Y represented in two's complement format using 6 bits. [2]

- CO1 A (e) Consider $(43)_x = (y3)_8$. What could be the possible values of x and y ? [2]

- R (f) Consider the following logic circuit whose inputs are functions f_1, f_2, f_3 and output is f . [2]

 

CO1

Given that
 $f_1(x,y,z) = \sum(0, 1, 3, 5)$,
 $f_2(x,y,z) = \sum(6, 7)$ and
 $f_3(x,y,z) = \sum(1, 4, 5)$, then determine f_3 .

Q.2 Attempt Any TWO from the following questions.



[12]

- A (a) Minimize the following boolean functions using algebraic manipulation [6]

CO2 $F_1 = abc'd' + abc'd + ab'c'd + abcd + ab'cd + abcd' + ab'cd'$
 $F_2 = AB + (AC)' + AB'C(AB + C)$

- CO2 A (b) Simplify the function $F(a,b,c,d,e,f) = \sum(6,9,13,18,19,25,27,29,45,47,61)$ by means of the tabulation method. [6]

- CO1 U (c) Consider the following circuit composed of XOR gates and non-inverting buffers. The non-inverting buffers have delays $\delta_1=2\text{ns}$ and $\delta_2=4\text{ns}$ as shown in the figure. Both XOR gates and all wires have zero delays. Assume that all gate inputs, outputs, and wires are stable at logic level 0 at time 0. If the following waveform is applied at input A, how many transition(s) (change of logic levels) occur(s) at B during the interval from 0 to 10 ns? Show the output at B. [6]

  

- Q.3 Attempt the following [12]
- CO2 A (a) Simplify the below Boolean expression using K-Map and implement with both Universal Gates. [6]
 $F(A,B,C,D) = A'B'C'D' + AC'D' + B'CD' + A'BCD + BC'D$
 Note: Both Normal and Complemented inputs are available.
- CO2 N (b) Simplify the below Boolean function along with the don't care conditions in both SOP and POS forms. [6]
 $F(w,x,y,z) = w'(x'y + x'y' + xyz) + x'z'(y + w)$
 $d = w'x(y'z + yz') + wyz$
- OR**
- Q.3 Attempt the following [12]
- CO2 A (a) Simplify the below function in both SOP and POS form using K Map. [6]
 $F(A,B,C,D) = (A' + B' + D')(A + B' + C')(A' + B + D')(B + C' + D')$
- CO2 N (b) Simplify and Implement the below Boolean expression using : [6]
 1. No more than 4 NAND gates
 2. No more than 3 NOR Gates
 $F(A,B,C,D) = AB' + ABD + ABD' + A'C'D' + A'BC'$