




DHARMSINH DESAI UNIVERSITY, NADIAD
FACULTY OF TECHNOLOGY
THIRD SESSIONAL
SUBJECT: (CE-308) Design of Digital Circuits

Examination	: B.Tech Semester III	Seat No.	:
Date	: 11-10-2023	Day	: Wednesday
Time	: 9:15 AM to 10:30 AM	Max. Marks	: 36

INSTRUCTIONS:


1. Figures to the right indicate maximum marks for that question.
2. The symbols used carry their usual meanings.
3. Assume suitable data, if required & mention them clearly.
4. Draw neat sketches wherever necessary.

 - Q1. Do as directed.** [12]
- CO3 A** (a) Q of the T flip-flop is zero. Clock transition from __ to __ when $T = \underline{\hspace{1cm}}$ will ensure flip-flop output Q' to have zero value. [2]




- CO3 U** (b) The flip-flop(s) which has not any invalid states is/are _____ [2]
(a) SR (b) JK (c) D (d) T
- CO3 U** (c) Why is state reduction important? [2]
(a) To save time of the designer (b) To reduce number of flip-flops
(c) To make the circuit attractive (d) To identify identical states
(e) To reduce complex states (f) All of these
- CO4 E** (d) If a counter having 10 FFS is initially at 0, what count will it hold after 2060 pulses? - [2]
Justify your answer.
- CO4 U** (e) Mention any two applications of Shift Register. [2]
- CO4 N** (f) The content of a 4 bit register is 1101. The register is shifted 6 times to the right with serial input being 101101. What will be the final content of the register? Explain your answer. [2]

 - Q2. Attempt Any TWO from the following:** [12]
- CO3 C** (a) Design an optimal sequential circuit for the following state diagram using JK flip-flop(s). [6]



 
- CO3 C** (b) (i) How many SR flip-flops will be required to implement the following counter? Justify your answer. [6]
00 - 11 - 00 - 01 - 10 - 00 - 11 - 00 - 11 - 00 - 01 - 10 - 00 - 11
- (ii) Draw state transition diagram for the given circuit.



- CO3 C** (c) Design a counter for the sequence: 0,1,3,2,4,5,2,7 and repeat. Use SR flip-flops. [6]

 Q3. Attempt the following:

- CO4 E (a) The circuit shown consists of J-K flip-flops, each with an active low asynchronous reset input (denoted by \bar{R}_d). Determine the counting sequence of the same, supporting it with the timing diagram. [12]




- CO4 C (b) Create a Mod 2N synchronous counter. Show the counting logic, state diagram, state table and timing diagram. [6]

OR

 Q3. Attempt the following:

- CO4 E (a) A mod-n counter using a synchronous binary up-counter with synchronous clear input (Synchronous clear is synchronized with the clock. It waits for a clock pulse to Reset FF output.) is shown in the figure. [12]



Determine the value of "n", and evaluate the counting sequence performed by the counter, supporting it with the timing diagram. [6]

- CO4 C (b) Design a Mod 5 asynchronous down counter that counts the sequence 7-6-5-4-3 using positive edge triggering as well as with negative edge triggering. [6]