



DHARMSINH DESAI UNIVERSITY, NADIAD

FACULTY OF TECHNOLOGY

THIRD SESSIONAL EXAM

SUBJECT: (ESC104) BASIC ELECTRICAL ENGINEERING (ICT)

Examination : B.Tech Semester I

Seat No. :

Date : 17/01/2023

Day : Tuesday

Time : 1 Hour and 15 Minutes

Max. Marks : 36

INSTRUCTIONS:

1. Figures to the right indicate maximum marks for that question.
2. The symbols used carry their usual meanings.
3. Assume suitable data, if required & mention them clearly.
4. Draw neat sketches wherever necessary.

Q.1 Do as directed.

- CO3 A (a) State True or False with proof, "The average power in pure capacitive circuit is $V_{rms}I_{rms}$." [12]
- CO3 U (b) A 120 volt ac source is connected across a pure inductor of inductance 0.70 H. If the frequency of the source is 60 Hz, Calculate the current passing through the inductor is _____. [2]
- [A] 4.55 amps, [B] 0.355 amps [C] 0.455 amps [D] 3.55 amps
- CO3 R (c) In LCR series circuit, the capacitance is changed from C to $4C$. For the same resonant frequency, the inductance should be changed from L to _____. (prove your answer) [2]
- [A] $4L$, [B] $L/2$ [C] $4L$ [D] $L/4$
- CO8 R (d) What are the Advantages of rotating field and stationary armature in alternator? [2]
- CO8 A (e) A 6-pole, 50 Hz, 3-phase, induction motor has rotor frequency 2 Hz. Find out slip and motor speed. [2]
- CO9 A (f) A 220 V, DC shunt machine has an armature resistance of 0.5 ohm. If the full-load armature current is 20 A, find the induced emf when machine act as (i) generator (ii) motor. [2]

Q.2 Attempt Any TWO from the following questions.

- CO8 A (a) A DC shunt motor takes an armature current of 110 A at 480 V. The armature circuit resistance is 0.2Ω . The machine has 6-poles and the armature is lap-connected with 864 conductors. The flux per pole is 0.05 Wb. Calculate (i) the speed and (ii) the gross torque developed by the armature. [12]
- CO8 A (b) A short-shunt compound generator delivers a load current of 20 A at 250 V, and has armature, series-field and shunt-field resistances of 0.05Ω , 0.30Ω and 200Ω respectively. Calculate the induced e.m.f. and the armature current. [6]
- CO8 A (c) An 8-pole DC shunt generator with 780 wave-connected armature conductors and running at 500 r.p.m. supplies a load of 10Ω resistance at terminal voltage of 250 V. The armature resistance is 0.2Ω and the field resistance is 250Ω . Find the armature current, the induced e.m.f. and the flux per pole. [6]

Q.3 Attempt Any ONE from the following questions.

- CO9 U (a) Explain the working operation of three phase induction motor and prove that it can never rotate at synchronous speed. [12]
- CO3 N (b) Two impedances given by $Z_1 = (10 + j5)$ and $Z_2 = (8 + j6)$ are joined in parallel and connected across a voltage of $V = 200 + j0$. Calculate the total current, its power factor and the branch currents. Draw the phasor diagram. [6]

OR

- CO9 U (a) Discuss split phase single phase induction motor with necessary diagram. [6]
- CO3 N (b) A coil of inductance 0.64 H and resistance 40Ω is connected in series with a capacitor of capacitance $12 \mu F$. Find: (i) The frequency at which resonance will occur. (ii) Q-factor of the circuit. (iii) The voltage across the coil and capacitor, respectively and also the supply voltage when a current of 1.5 A at the resonant frequency is flowing. [6]